

1. For any text of inputs, A and B , the following circuits give the same output, Q , expect oone. Which one is it?

